

Figure 1: The Set-Reset Flip Flop

NOW				NEXT		
S	R	P _t	Q _t	P _{t+1}	Q _{t+1}	
1	1	0	0	1	1	Unstable
1	1	0	1	0	1	Stable
1	1	1	0	1	0	Stable
1	1	1	1	0	0	Unstable

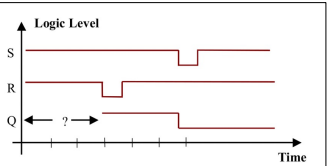


Figure 2: The Set-Reset Flip Flop Timing

Combinatorial: output is a combination of **only inputs**

Sequential: output is a combination of **inputs and previous outputs** (we need a transition table or state diagram, it needs some notion of time)

Asynchronous: output will have correct value after an **undefined** amount of time

Synchronous: output will have correct value after a **defined** amount of time (a clock signal tells us time)

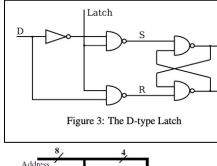


Figure 3: The D-type Latch

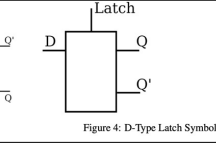


Figure 4: D-Type Latch Symbol

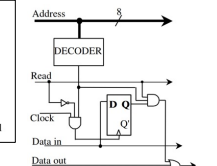


Figure 1: One bit of static RAM

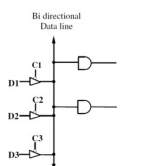


Figure 2: Tri-State Buffering

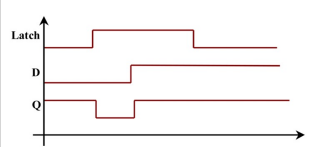


Figure 5: A Spike in the D-Type Latch

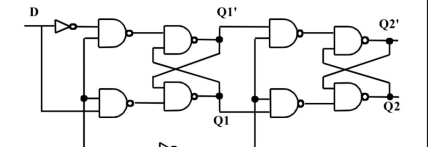


Figure 6: The master-slave D-Type flip flop

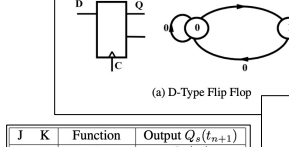


Figure 3: Layout of RAM

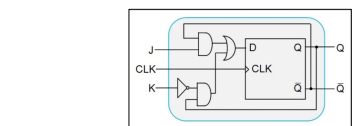


Figure 1: One bit of static RAM

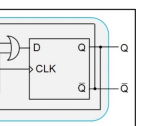


Figure 2: Tri-State Buffering

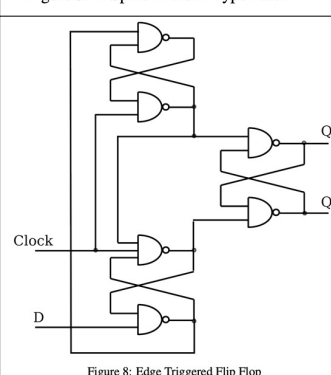


Figure 8: Edge Triggered Flip Flop

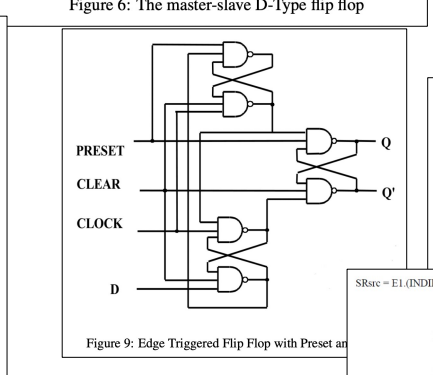


Figure 9: Edge Triggered Flip Flop with Preset and Clear

J	K	Function	Output $Q_s(t_{n+1})$
0	0	No Change	$Q_s(t_n)$
0	1	Reset	0
1	0	Set	1
1	1	Toggle	$Q'_s(t_n)$

Figure 3: J-K Flip Flop



Figure 3: J-K Flip Flop

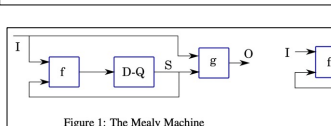


Figure 1: The Mealy Machine

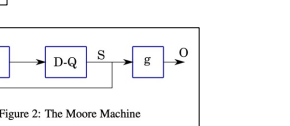


Figure 2: The Moore Machine

